







Operator	Logic Gate		Example			Rule
NOT		\overline{A}	INPUT		OUTPUT	Invert
			A		NOT A	
			0		1	
			1		0	
AND		$A.B$	INPUT		OUTPUT	Both A and B = 1 → 1 Anything ELSE → 0
			A	B	A AND B	
			0	0	0	
			0	1	0	
			1	0	0	
			1	1	1	
NAND		$\overline{A.B}$	INPUT		OUTPUT	Both A and B = 1 → 0 Anything ELSE → 1
			A	B	A AND B	
			0	0	1	
			0	1	1	
			1	0	1	
			1	1	0	
OR		$A+B$	INPUT		OUTPUT	Either A or B = 1 → 1 Anything ELSE → 0
			A	B	A AND B	
			0	0	0	
			0	1	1	
			1	0	1	
			1	1	1	
NOR		$\overline{A + B}$	INPUT		OUTPUT	Both A and B = 0 → 1 Anything ELSE → 0
			A	B	A AND B	
			0	0	1	
			0	1	0	
			1	0	0	
			1	1	0	
XOR		$A \oplus B$	INPUT		OUTPUT	Either A or B = 1 → 1 Excludes BOTH being 1
			A	B	A AND B	
			0	0	0	
			0	1	1	
			1	0	1	
			1	1	0	

Logic Gate Table